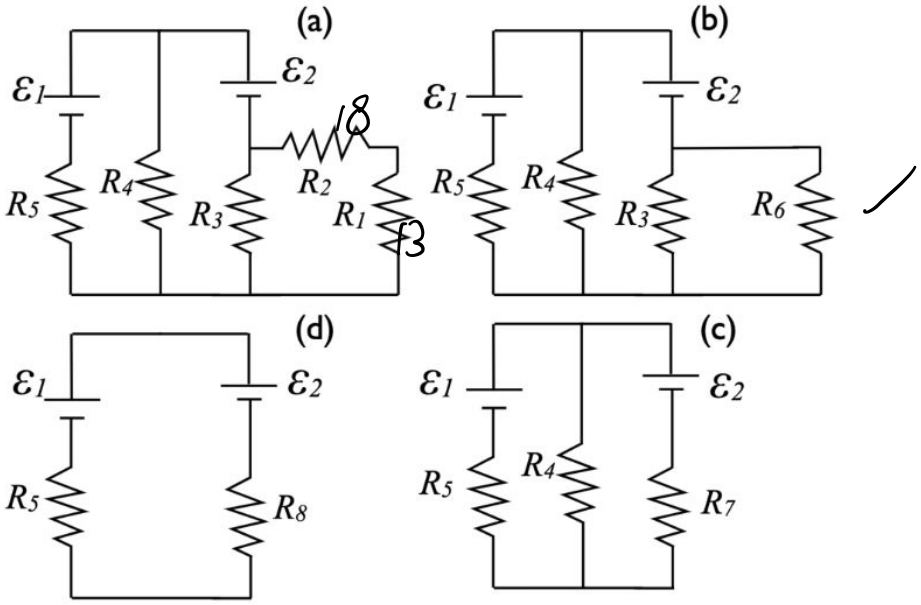
## 2 P650-1 - Resistor Circuit Reduction [Total: 1]

A car battery charger circuit contains resistors with resistances $R_1 = 13\Omega$, $R_2 = 18\Omega$, $R_3 = 20\Omega$, $R_4 = 10\Omega$, $R_5 = 7\Omega$. The circuit is reduced in the steps shown in the figure below.




**Part 1** [1]

Select the steps in reducing the circuit that are allowed.

A. $(a)$ to $(b)$

B. $(b)$ to $(c)$

C. $(c)$ to $(d)$